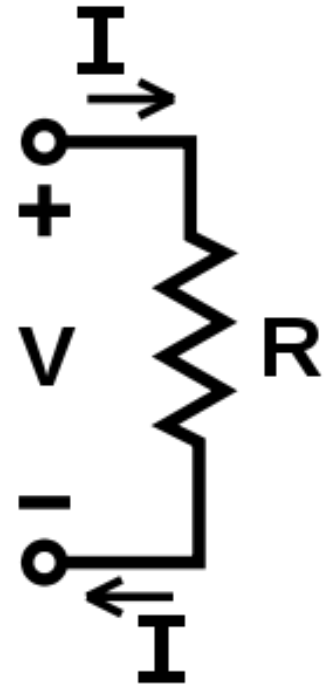



Ohm's Law

$$V = I \cdot R$$

- **V** is **Voltage Drop**, the **Potential Difference** between two ends of a wire (or resistor, light bulb etc). Measured in **Volts [V]**
- **I** is **Electric Current**, the total charge flowing through the wire in 1 sec. Measured in **Amperes [A]** (Coulomb per second) : **1A=1C/s**
- **R** is **Resistance** of the wire. Measured in **Ohms [Ω]**. **1Ω=1V/A**



Serial and Parallel Circuits

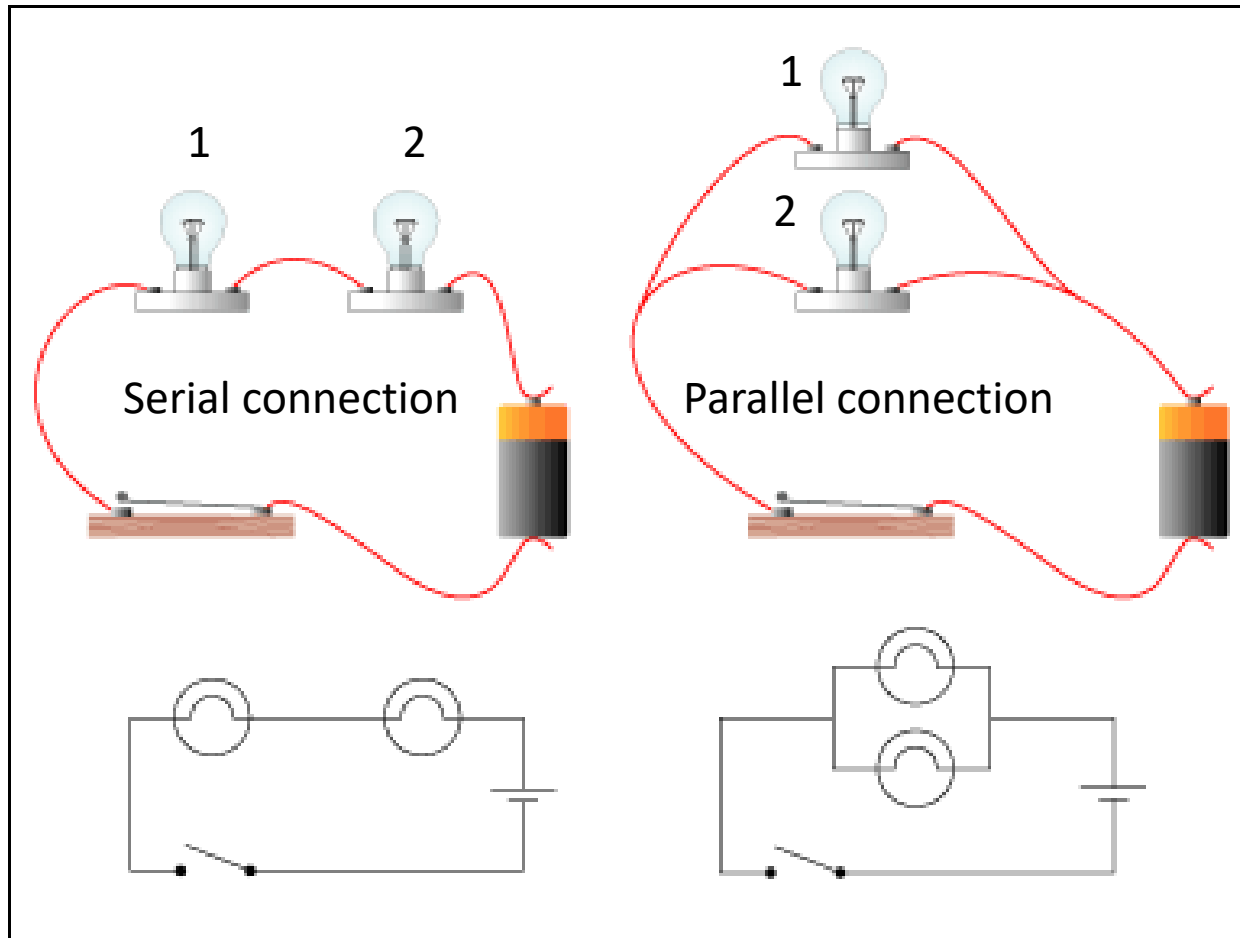

Serial:

- Currents are the same: $I_1 = I_2$
- Voltage is added: $V = V_1 + V_2$

Parallel:

- Currents are added: $I = I_1 + I_2$
- Voltages are the same: $V_1 = V_2$

Homework

Problem 1

An electric heater is made out of a piece of wire with resistance $R = 10 \Omega$, plugged into a standard 110V outlet. Find the current through this wire, and the overall power of this heater (remember that $\text{Power} = V \cdot I$).

Problem 2

Two resistors, 10Ω and 20Ω are connected to a 1.5V battery in parallel. Sketch the circuit, and find the total current flowing via the battery.

You want to replace these two resistors with a single one, so that the current stays the same. How large should be its resistance?