

Homework 12

Nodal analysis problems.

In the circuits below find current I shown in red:

