

MATH 8B [2024 NOV 10]
HANDOUT 8 : LOGIC 3 : SR FLIP-FLOP. CONDITIONALS.

SR FLIP-FLOP


Today we will play a little more with circuits. So far we have dealt with *combinational circuits*. Such a circuit C takes in some inputs, uses some combination of gate, and implements a logic function $f_C(x_1, \dots, x_n)$ purely of the inputs x_1, \dots, x_n . (More generally, it may have multiple outputs corresponding to m Boolean functions $f_{C,1}, \dots, f_{C,m}$.)

Now, we're going to look at a slightly more complicated type of circuit - a *sequential circuit*, for which the output does not only depend on the inputs, but also on the previous inputs (or state of the system). These are said to have memory.


A simple example of such a circuit is the following, which is called SR Flip-Flop. Interestingly, the output of NAND -gates is also an input to other NAND -gates. Let us look at how it works.

Let's imagine that we turn S on to 1. The NOT -gate changes it to 0, and when it is fed to the NAND gate, the output of it would be 1, since $0 \text{ NAND } X = 1$ for any X (make sure you understand why it is so!). As a result, the Q bulb will turn on.

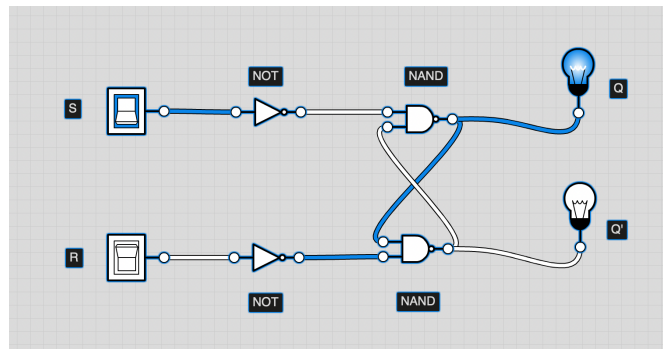
At the same time, R is off (is 0), and it is changed to 1 by the NOT -gate, and fed to NAND along with the output of the top NAND -gate, so the output of the bottom NAND -gate is 0 (since $1 \text{ NAND } 1 = 0$).



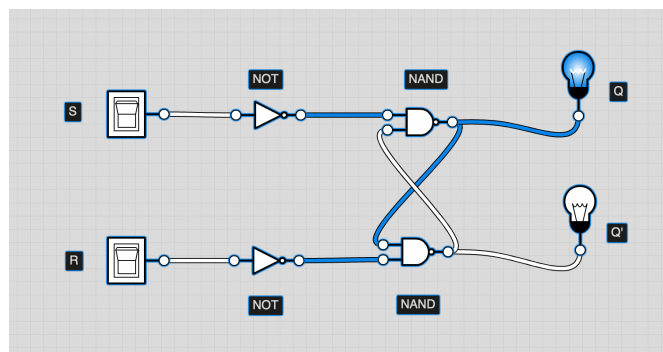
Interestingly, if we now flip S back off, the lightbulbs will not change their state: lightbulb Q will stay on, and Q' will stay off: one of the inputs to the top NAND will always stay off, regardless of what S is.



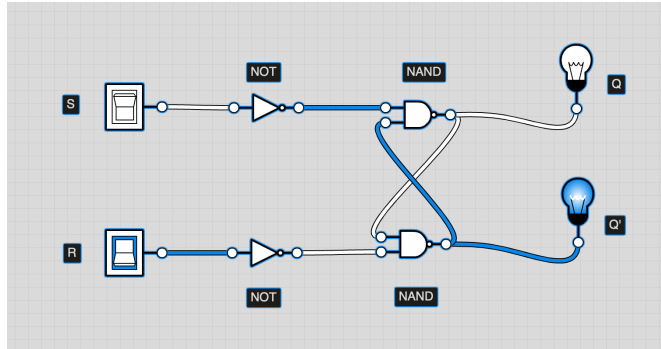Now if we switch S to off, and turn R on, the lightbulbs will flip: Q' will be lit up, and Q will be off.



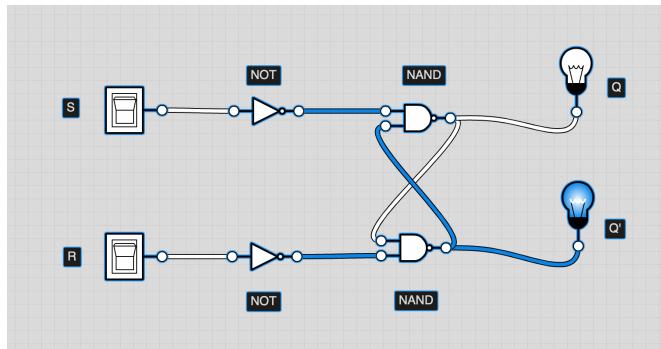We will also observe a similar situation: now switching R to off will not change the state of lightbulbs:



The state when the top lightbulb is lit up is called S-state, that is the flip-flop is in SET position. When the lower lightbulb is on, the flip-flop is in RESET (R) position.

A simple way to summarize the working of this circuit is: when the reset R is on, then toggling S will flip the state of Q (to be the same as S). So it allows us to reset the main output (the set state Q). When the reset R is off, then Q turns on (if it not already on) as soon as the set input S comes on, and stays on after that, until we reset again.

The interesting thing about this circuit is that it has **memory**: once it's in the SET-state, the top lightbulb indicates it, and switching S-switch off won't change anything – the top lightbulb will still be on. Similarly, once we're in R-state, we can switch the R-switch off, but the lightbulbs will still indicate that we are in the R-state (the 2nd light bulb is on)

REVIEW: IMPLICATION AND EQUIVALENCE

Recall the implication or conditional operator \Rightarrow , which has the truth table

A	B	$A \Rightarrow B$
T	T	T
T	F	F
F	T	T
F	F	T

Note that in particular, in all situations where A is false, $A \Rightarrow B$ is automatically true. E.g., a statement “if $2 \times 2 = 5$, then...” is automatically true, no matter what conclusion one puts in place of dots.

We showed that it is equivalent to $\neg A \vee B$.

We also looked that the equivalence operator \Leftrightarrow , defined as: $(A \Leftrightarrow B)$ is true if A, B always have the same value (both true or both false). We showed last homework that it is the same as $(A \Rightarrow B) \wedge (B \Rightarrow A)$. We also saw that it is the same as $\neg(A \text{ XOR } B)$.

PROBLEMS

1. Show that $A \Rightarrow B$ is not equivalent to $B \Rightarrow A$, i.e. they have different truth tables and one of them can be true while the other is false.
2. Prove the contrapositive law: $A \Rightarrow B$ is equivalent to $(\neg B) \Rightarrow (\neg A)$
3. Can you rewrite $\neg(A \Rightarrow B)$ without using the implication operation?
4. Consider the following statement (from a parent to his son):
 "If you do not clean your room, you can't go to the movies"
 Is it the same as:
 - (a) Clean your room, or you can't go to the movies
 - (b) You must clean your room to go to the movies
 - (c) If you clean your room, you can go to the movies
5. English language (and in particular, mathematical English) has a number of ways to say the same thing. Can you rewrite each of the verbal statements below using basic logic operations (including implications), and variables
 - A : you get score of 90 or above on the final exam
 - B : you get an A grade for the class
 (As you will realize, many of these statements are in fact equivalent)
 - (a) To get A for the class, it is required that you get 90 or higher on the midterm
 - (b) To get A for the class, it is sufficient that you get 90 or higher on the midterm
 - (c) You can't get A for the class unless you got 90 or above on the final exam
 - (d) To get A for the class, it is necessary and sufficient that you get 90 or higher on the midterm
6. Show that in all situations where A is true and $A \Rightarrow B$ is true, B must also be true. [This simple rule has a name: it is called *Modus Ponens*.]
7. Show that if $A \Rightarrow B$ is true, and B is false, then A must be false. [This is called *Modus Tollens*.]
8. Is $A \Rightarrow (B \Rightarrow C)$ the same as $(A \Rightarrow B) \Rightarrow C$?
9. Show that $A \Rightarrow (B \Rightarrow C)$ the same as $(A \wedge B) \Rightarrow C$.
10. Fill in the following table with True/False values:

	Commutative	Associative
AND		
OR		
XOR		
NAND		
\Rightarrow		
\Leftrightarrow		