
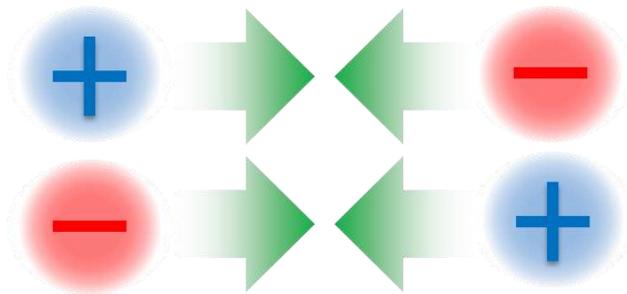


Electric charge.

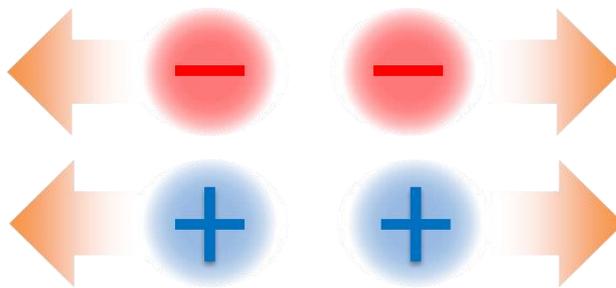

Different signs: attraction



Same signs: repulsion

Charge unit in SI is "Coulomb" or just "C"

Charge conserves: it cannot be created or destroyed

Electric potential. Voltage.




Voltage source (Battery)



Alessandro Volta (1745-1827)

If you look at an electrical battery, you will see, that one end is marked with a “+”, the other one – with “-”. This means that the “+” end has positive charge, while the other end has equal, but negative charge. Total charge of the battery is zero. So, any object, charged positively will be repelled from the “+” end and will be attracted to the “-” end. You can say that a positively charged object will have *more* electrostatic potential energy at the “+” end than at the “-” end. Similarly, a ball at the top of a hill has more gravitational potential energy than same ball at the foot of the hill and “wants” to roll down.

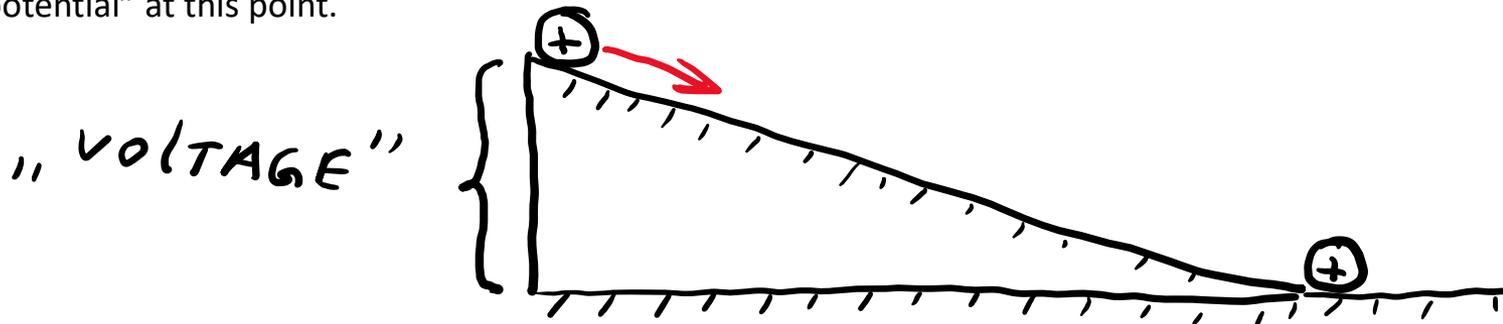Electrostatic potential energy per unit charge in a certain point is called “electrostatic potential” or just “potential” at this point.




Potential difference between points A and B – “ V_{AB} ” is called voltage drop between A and B.
This name is given after Italian physicist Alessandro Volta (1745-1827)

V_{AB} is equal to the work done by the electric force on a unit charge when the latter is moved from point A to point B.

Electric current

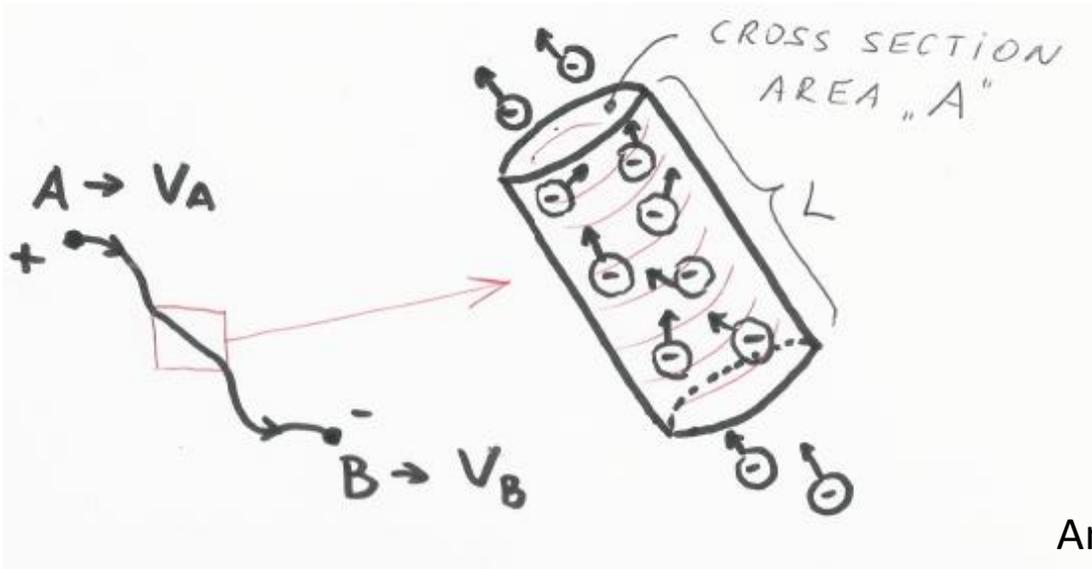Electric current is displacement of charge




Andre-Marie Ampere (1775-1836)

Electric current magnitude I is equal to the charge passing through the cross section of the Wire per unit time.

$$[I] = A \text{ (Ampere)} = \frac{\text{Coulomb}}{\text{second}}$$

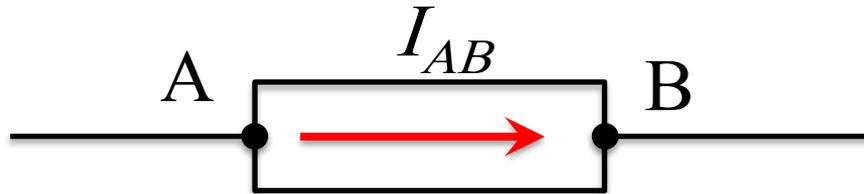Electric current flowing through a circuit element



$$I_{AB} = -I_{BA}$$

By definition, the direction of the current is the direction of flow of the positive charge



Electrical neutrality:

charge, entering at one end (Δq_{in}) = charge, exiting at the other end (Δq_{out})

$$I_{in} = I_{out}$$

Resistance. Ohm's law




Georg Simon Ohm
(1789-1854)

$$\text{Ohm's law: } V = R \cdot I$$

Resistance of the wire with a length L
and a cross section area A :
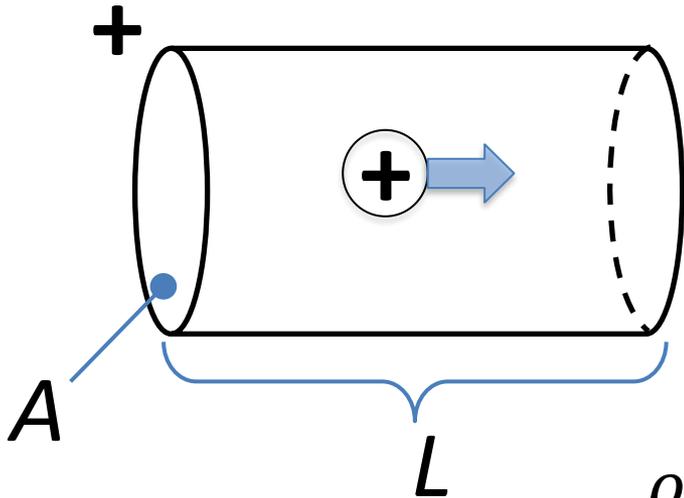
$$R = \frac{\rho L}{A}, [\text{Ohm, or } \Omega]$$



ρ is the resistivity of the wire material

Ideal wire



$$R=0$$

$$V_{AB} = R \cdot I_{AB} = 0 \cdot I_{AB} = 0$$


If two points are connected with an ideal wire then the voltage between these point is zero, no matter what else is connected to these points.

Resistor



Power, delivered to resistor:
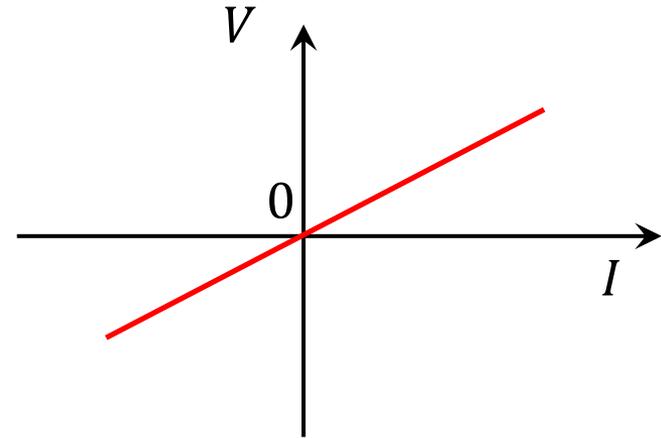
$$P = V \cdot I = I^2 \cdot R = \frac{V^2}{R} > 0$$




$$\text{Slope} = R = \frac{V}{I}$$




Resistor is a passive element. Energy, delivered to an ideal resistor is immediately converted (“dissipated”) to heat. No electrical energy is stored.

Parallel and series connection of resistors

Series connection

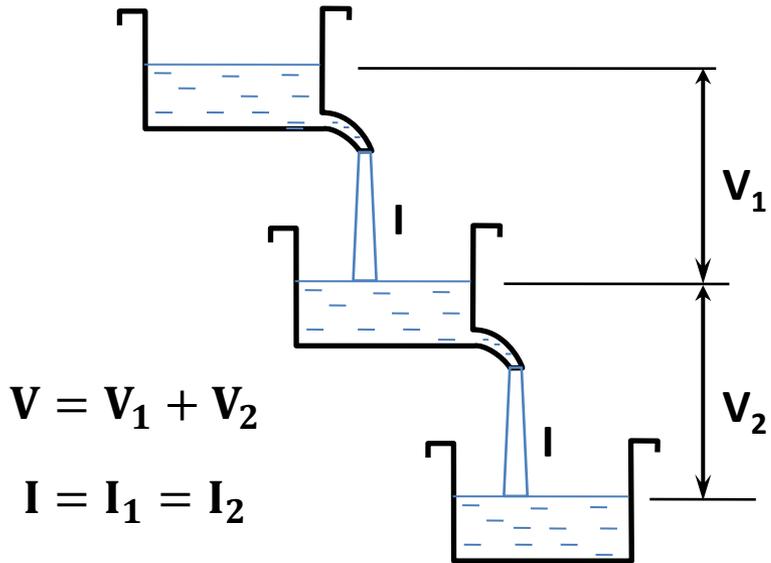


Parallel connection

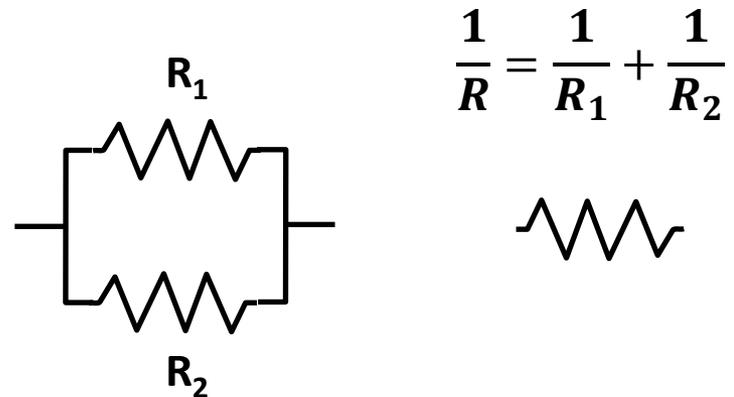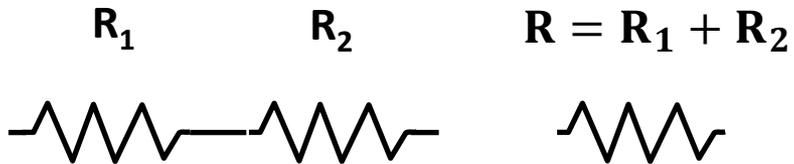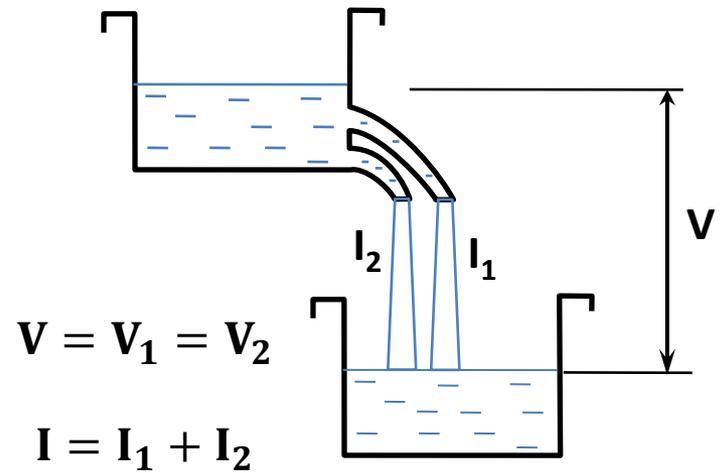

Problems:

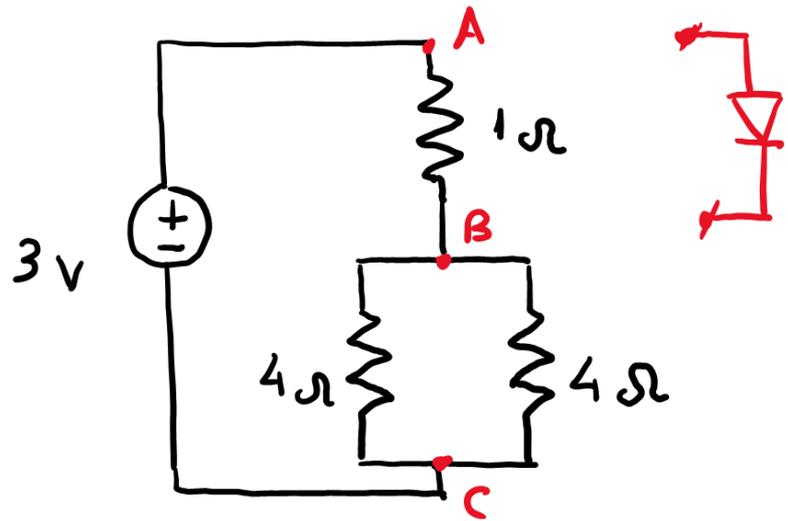1. The light emitting diode (shown in red in the Figure below) opens at 1.5V. Will it emit the light if you connect it to points A and B? What about B and C?



Problems:

1. Two light emitting diodes (red and green) are connected as shown in Figure below. Both diodes open at the same voltage V_{opening} . Will they emit the light? What happens if we will change the polarity of the voltage source?

