

Teacher: Sayan Chakraborti

Student:

Adding Resistances

Question 1:

There are 2 charges in series, their resistances are 100 Ohms and 10 Ohms. What's the total resistance? Is it similar to the smaller or larger resistance?

Question 2:

Now imagine they are in parallel. What's the total resistance? Is it similar to the smaller or larger resistance this time?