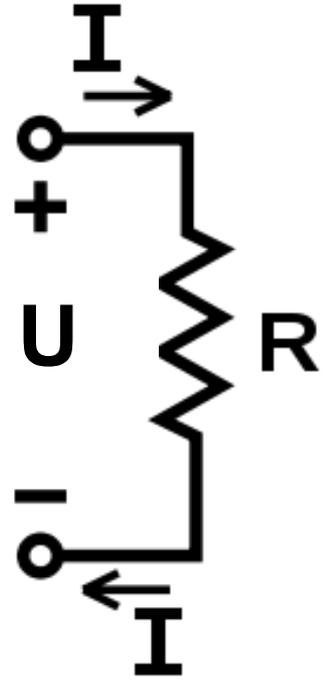


# Ohm's Law

$$V = I \cdot R$$

- **V** is **Voltage**, the **Potential Difference** between two ends of a wire (or resistor, light bulb etc). Measured in **Volts [V]**
- **I** is **Electric Current**, the total charge flowing through the wire in 1 sec. Measured in **Amperes [A]** (Coulomb per second) :  
**1A=1C/s**
- **R** is **Resistance** of the wire. Measured in **Ohms [ $\Omega$ ]**. **1 $\Omega$ =1V/A**



## Serial connection:


Current the same. Voltage adds up.

$$I_{total} = I_1 = I_2 = I_3$$

$$U_{total} = U_1 + U_2 + U_3$$

the circuit can be replaced with an single resistor :
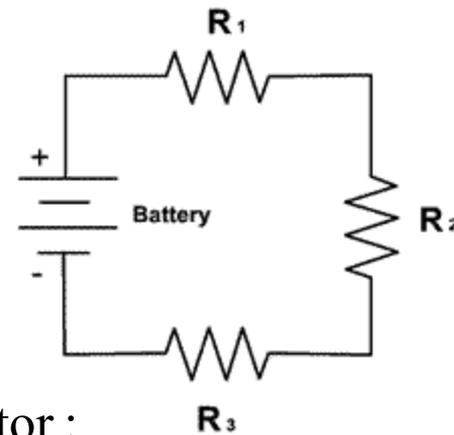
$$R = \frac{U_{total}}{I_{total}} = R_1 + R_2 + R_3$$




## Parallel connection:

Voltage the same. Current adds up.

$$U_{total} = U_1 = U_2 = U_3$$

$$I_{total} = I_1 + I_2 + I_3$$
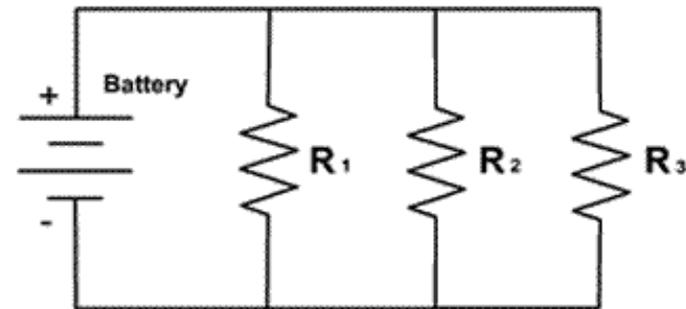
$$\frac{1}{R} = \frac{I_{total}}{U_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



# POWER

$$Power = \frac{Work}{time}, \quad P = \frac{\Delta W}{\Delta t}$$

- **W** may be mechanical work, or work done by a battery driving an electric current.
- In this definition, **Work** can also be replaced with **Heat**. That will be thermal power rather than mechanical or electric one.
- Units of power are Watts [W]: 1W=1J/s (Joule per second)

## POWER IN ELECTRIC CIRCUIT

$$Power = Current \times Voltage, \quad P = I \cdot V$$

# Homework

**Problem 1.** Derive expression for Power  $P$  consumed by a resistor or a light bulb with resistance  $R$ , for two cases : (a) you know the current  $I$  flowing through it, (b) you know the voltage  $V$  applied to it.

**Problem 2.**

A light bulb has power  $P= 100$  W when plugged into 110 Volt outlet. Find the total power of three such light bulbs, when they are plugged into the same outlet

- a) in parallel,
- b) in series.

**Problem 3**

An electric motor is used to lift a load of mass  $m=50$  kg to height  $h=10$ m , over time  $t=10$ s  
Find the power of the motor and current that runs through it, if the voltage on the motor is  $V=110$ V.