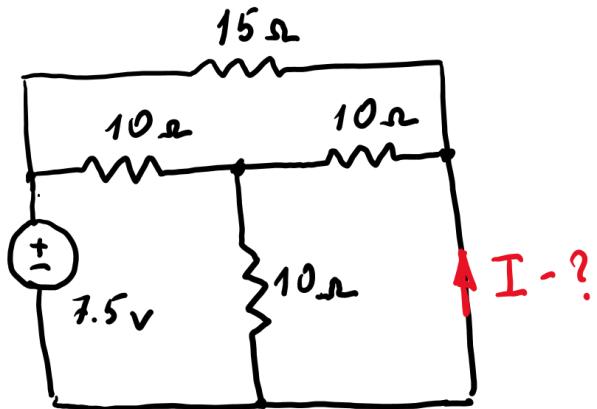


## Homework 10

Find current  $I$  in 2 circuits below:

*Hint: remember, that if 2 nodes are connected with the ideal wire they have same potential.*

a)



b)

