

Homework 25.

Think over the following problems:

1. Find equivalent resistance of the circuit below:



2. Find voltages in the circuits below:

